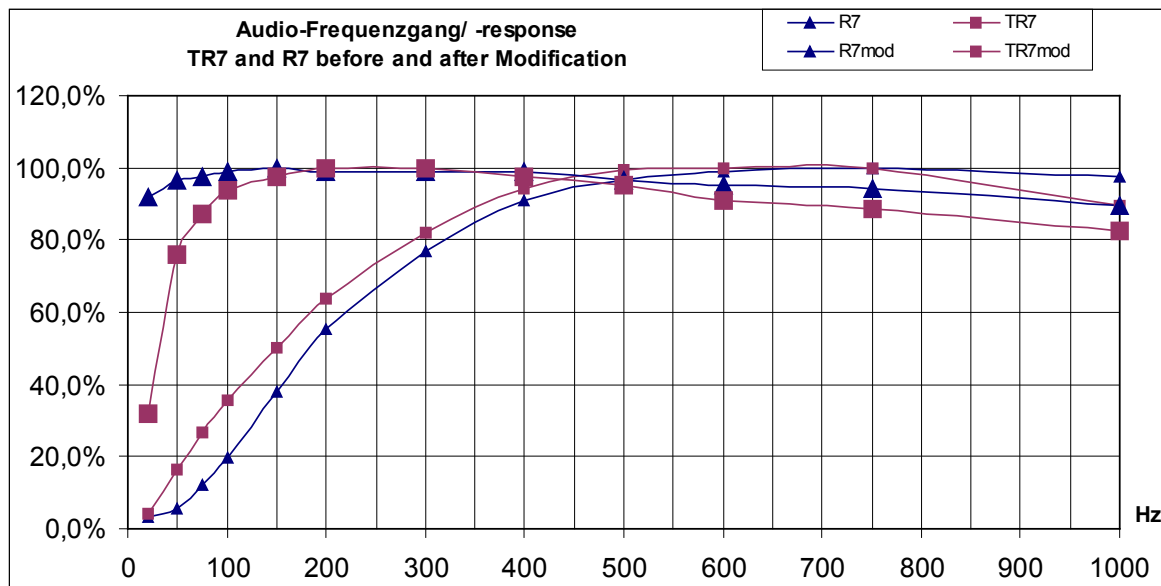


## Modification of RX-Audio-Response for 7-Line (TR7 and R7)

### Introduction

My 7-Line had a rather weak audio at low frequencies, even with „big“ speakers. I'm sure, that the developing engineers have designed the audiocircuits to increase higher frequencies for a better readability, but it is a question of individual feeling. First, i made some measurements.



Picture 1 AF-Response of TR7 and R7 before and after Modification

These AF-measurements were made in mode AM; my TR7/R7 have AM-filters with 6kHz/4kHz. A 14MHz-signal was taken from a signal generator type HP8640B in Mode AM with  $m=80\%$  and it was levelled over the receivers AGC's thresholds. The modulating AF was varied from 20Hz to 1kHz - holding  $m$  konstant at 80%. The AF-output was measured at the speakers-jack with an AF-voltmeter type HP400E – parallel with 4 Ohms simulating the external speaker.

Result: A strong damping of frequencies below 400Hz can be seen in picture 1 (curves with small dots). The y-axis is calibrated in  $mV_{rms}$ , and related in percentage to the maximum voltage within the range of frequencies.

Reason: Examining the AF-circuits, it can be seen, that there are coupling capacitors, which are too small. Increasing these capacitors solve this problem.

#### Modifications:

The modifications described in this article lead to the curves with the big dots in picture 1. All capacitors with 0,47uF are non polarised/monolithic; capacitors with 4u7 or bigger are electrolytic (observe polarity!).

Note 1: Don't use a speaker as load, because it's mechanical resonance (between 20 and 100Hz) will have a strong influence on the result at these frequencies!

Note 2: Don't use the R7-phonjack at the front, because there is an internal series resistor of 220 Ohms. Use the jack for the external speaker at the rear.

## RX-Audiocircuit of TR7

Table 1, Picture 2 and 3 show the modified C's on the TR7's board „2ndIF/AGC“ and the locations.

Capacitor	Old value	New value
C 1140	1uF	4u7 or 10uF/15V
C 1146	1uF	4u7 or 10uF/15V
C 1147	22uF	100uF/25V
C 1150	0,05uF	0,47uF
C 1151	22uF	100uF/25V
C 1152	0,01uF	0,47uF
C 1159	250uF	1000uF/25V
C 1166	1uF	4u7 or 10uF/15V

Table 1 Modified values TR7 - 2ndIF/Audio

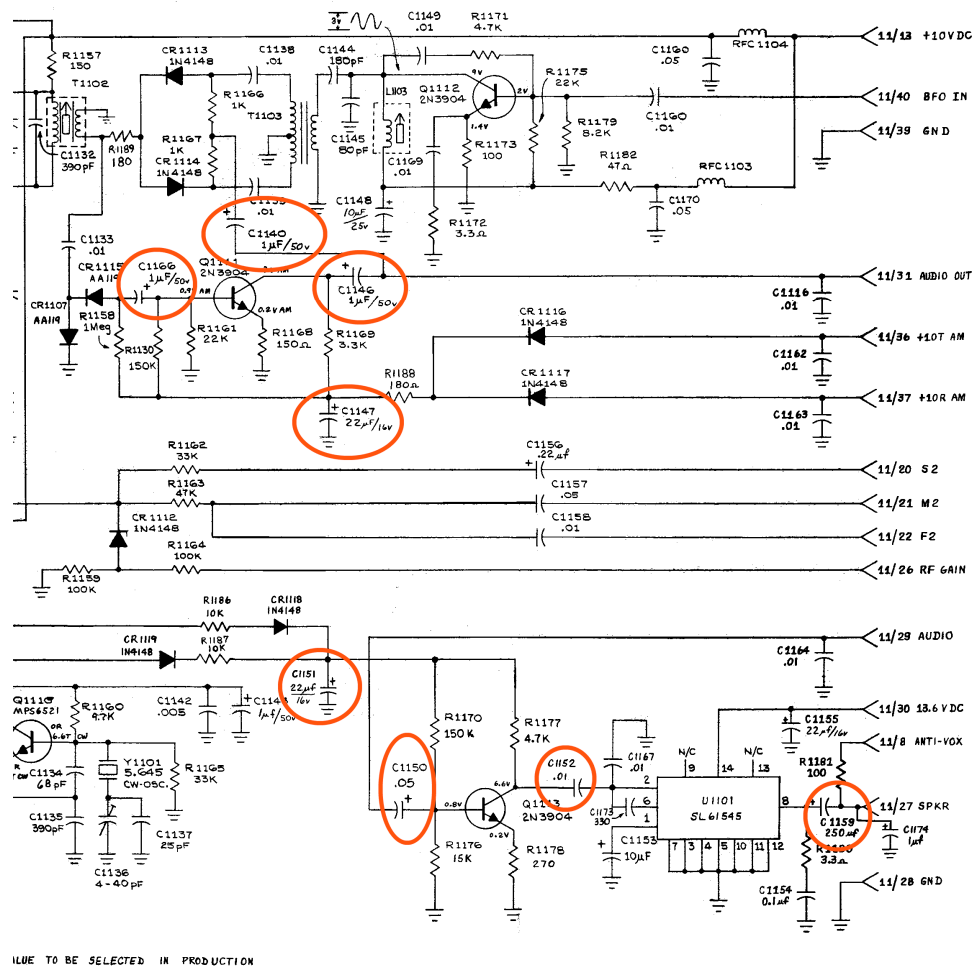


Fig. 2-22 2nd IF/Audio Board Schematic

2-63

Picture 2 Modified C's on the TR7 – 2<sup>nd</sup> IF/Audio Board

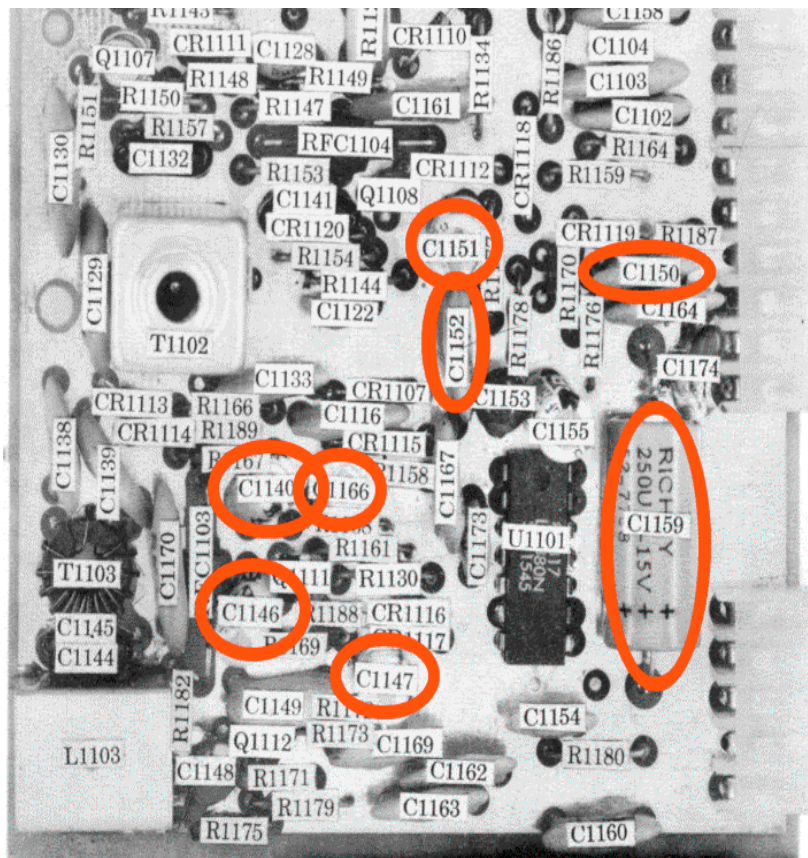


Fig. 2-21 2nd IF/Audio Board Pictorial 2-63

Picture 3 Location on the TR7 – 2<sup>nd</sup> IF/Audio Board

### RX-Audiocircuit of R7

Table 2, Picture 4 and 5 show the modified C's on the R7's board „Audio/PTO Buffer“ and the locations.

Capacitor	Old value	New value
C 306	0,05uF	0,47uF
C 316	0,05uF	0,47uF

Table 2 Modified values R7 - Audio/PTO Buffer


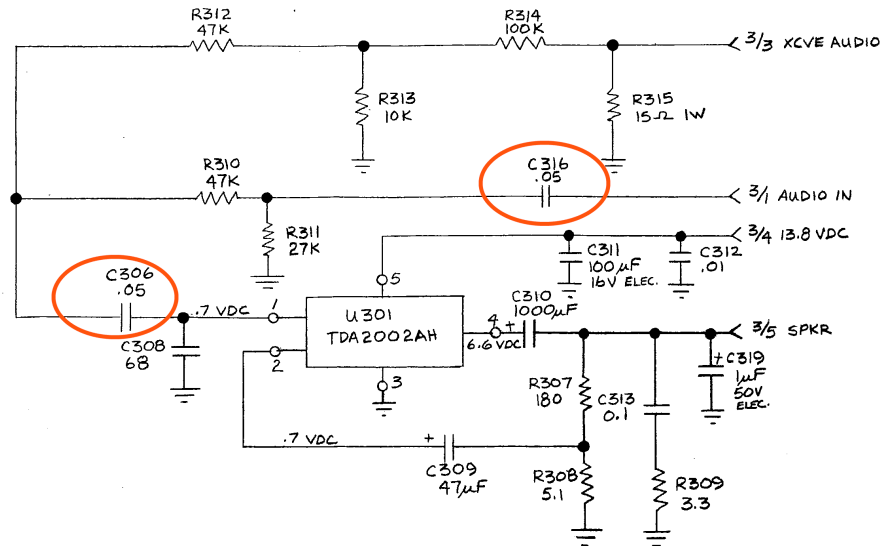


Fig. 2-6 Audio/PTO Buffer Board Schematic

2-16

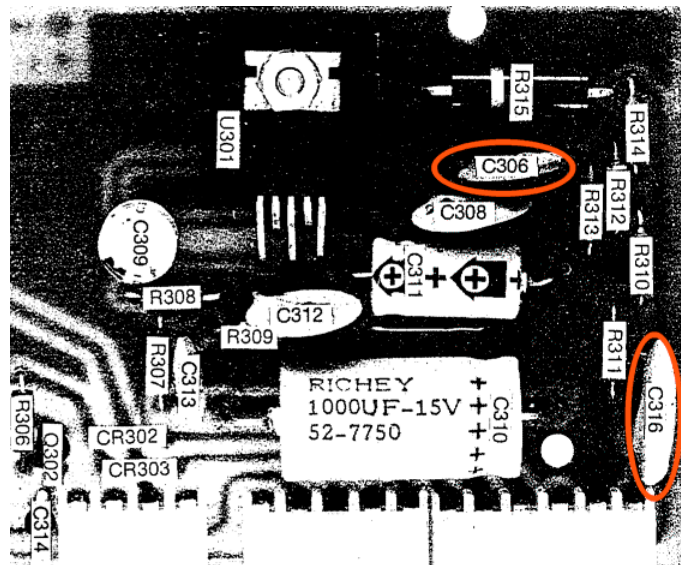Picture 4 Modified C's on the R7 - Audio/PTO Buffer



Picture 5 Locations on the R7 Audio/PTO Buffer

Table 3, Picture 6 and 7 show the modified C's on the R7's board „2<sup>nd</sup>/3<sup>rd</sup> IF/AGC“ and the locations.

Capacitor	Old value	New value
C 1147	0,47uF	10uF/63V
C 1153	0,05uF	0,47uF

Table 3 Modified values R7 - 2<sup>nd</sup>/3<sup>rd</sup> IF/AGC


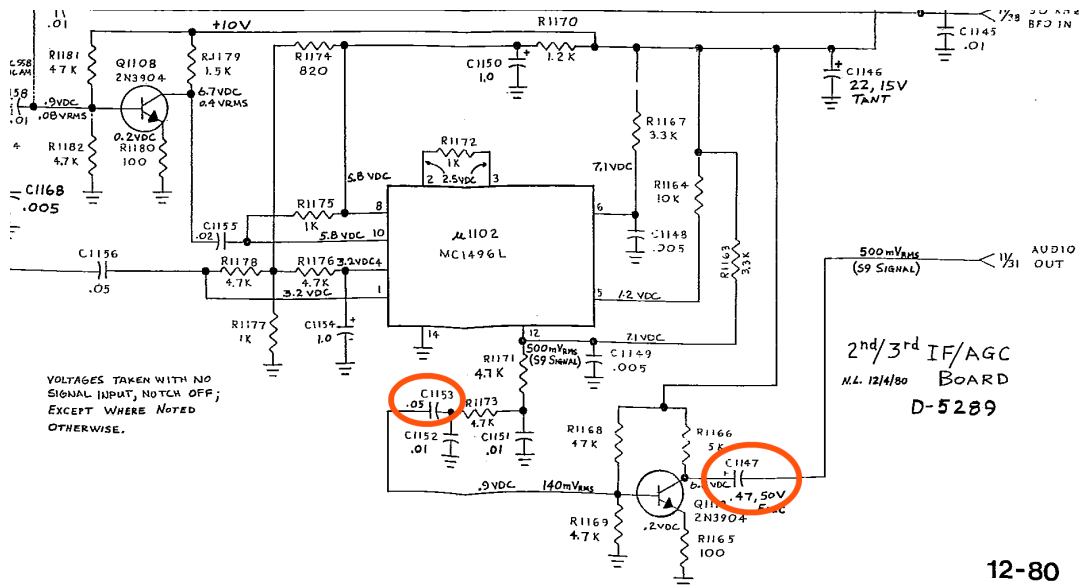


Fig. 2-22 2<sup>nd</sup>/3<sup>rd</sup> IF/AGC Board Schematic

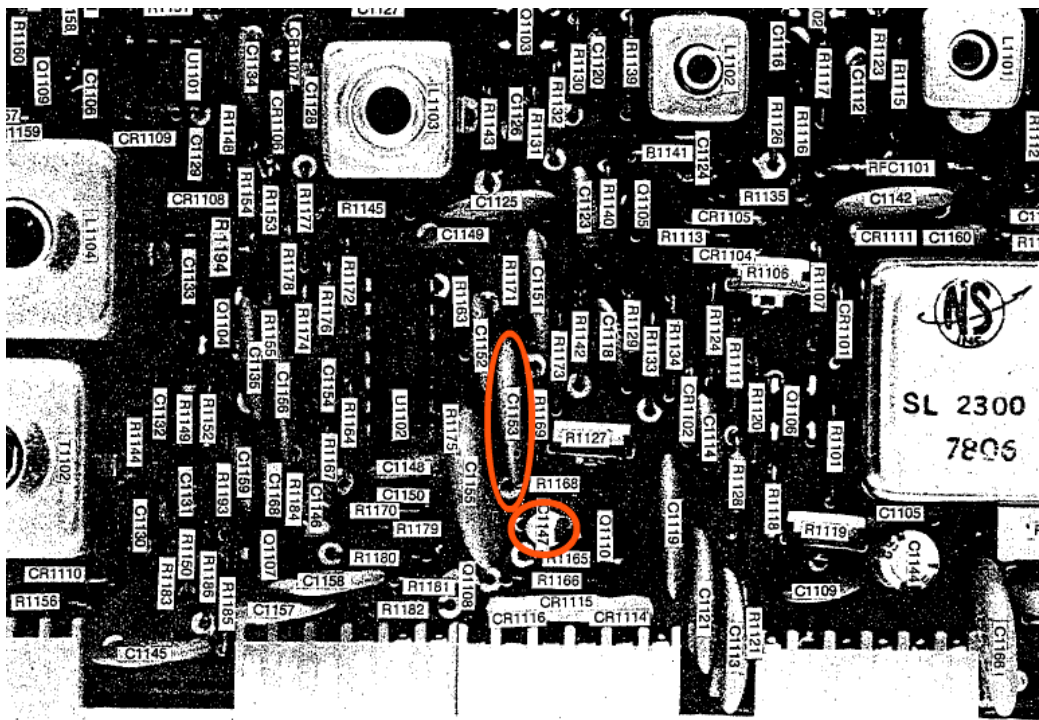12-80  
2-59

Picture 6 Modified C's on the R7 - 2<sup>nd</sup>/3<sup>rd</sup> IF/AGC Board



Picture 7 Locations on the R7 - 2<sup>nd</sup>/3<sup>rd</sup> IF/AGC Board

If you want to contact the author:  
Stefan Steger, DL7MAJ, eMail: [dl7maj@darf.de](mailto:dl7maj@darf.de)  
Homepage: [www.dl7maj.de](http://www.dl7maj.de)