

## Modification of the HV-Circuits of HP 8614 and 8616

First of all:

Voltages higher than 50VDC may be lethal! This article describes circuits operating with voltages up to more than 700 (sevenhundred) volts!

This may be immediately lethal!

Don't continue reading if you have not sufficient knowledge and experience to handle such circuits.

---

*You're still reading? Welcome and let's start.*

The HP8614 and HP8616 are GHZ-generators from 0.8 to 2.4GHz (8614) and from 1.8GHz to 4.5GHz (8616) equipped with klystrons 6BL6 and 6BM6.

On flea markets I acquired two 8614's and one HP8616. They worked as promised by the sellers but the output was rather noisy and showed a lot of hum. The source of the trouble was quickly found: The DC-supplies of the klystron (320VDC and 720VDC) had a ripple of > 10Vpp and other random noise.

The reasons were:

1. Bad electrolytic capacitors in the HV-DC-supply
2. Maybe some dying tubes in the HV-regulating circuits

Had no new tubes available and on the other hand I wanted to reduce the heat dissipation inside the generators. So I decided to design a new HV-circuit for these generators to replace the old tube-based voltage-regulator by a modern transistor-based circuit.

Using some BUZ80A's, the circuit is a transistorized mirror of the original tube-circuit /1/ and supplies the -212VDC, -320VDC and -720VDC (8616) / -670VDC (8614) including the 6.1VDC filament supply (picture 1).


The internal square-wave generator (1kHz) is replaced by a TTL-based circuit with a bigger tuning range from app. 400Hz to 3kHz (picture 2).

Note: The pin numbers in the new circuits are identical to the original circuits and have to be connected 1:1.


Picture 3 is the original inside view showing the tube-based HV-circuit.

The following pictures 4 to 13 show the modification step by step.

Page 2 from 9

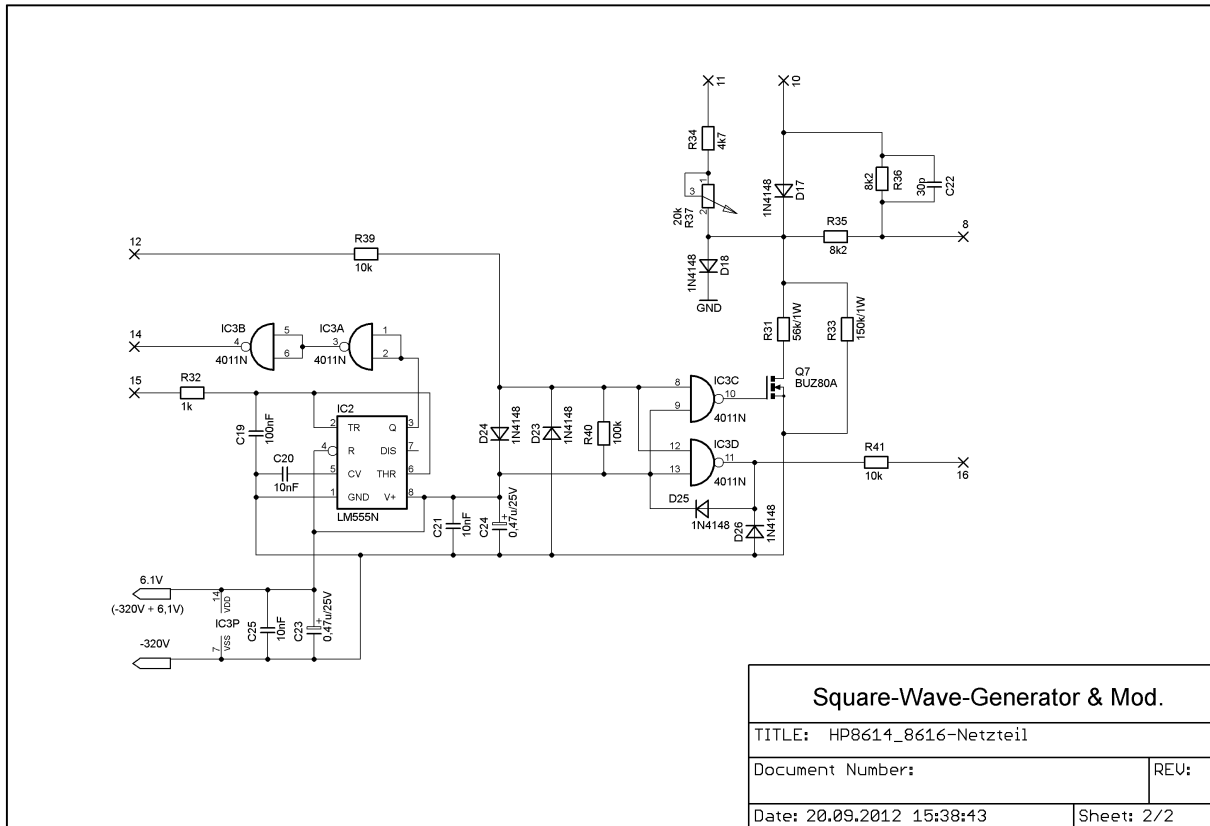


Picture 2: Square-wave-generator

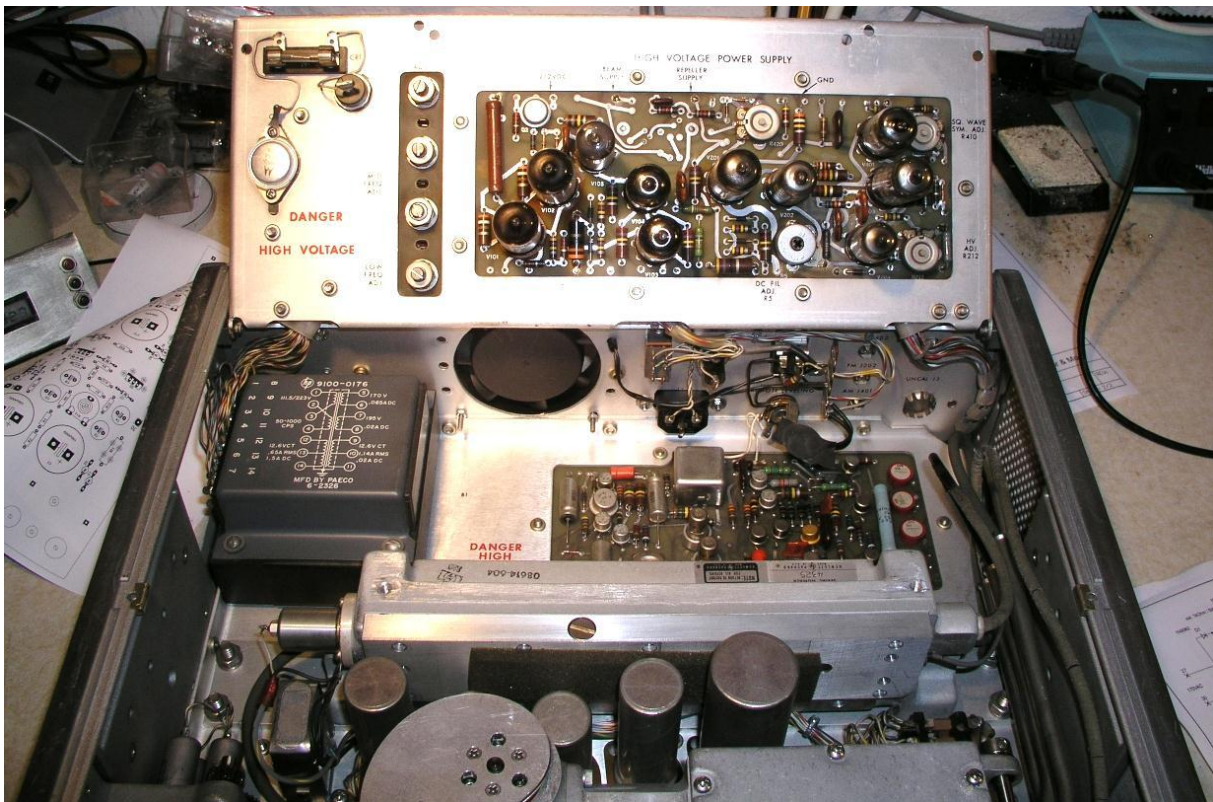


Picture 3: Original inside view



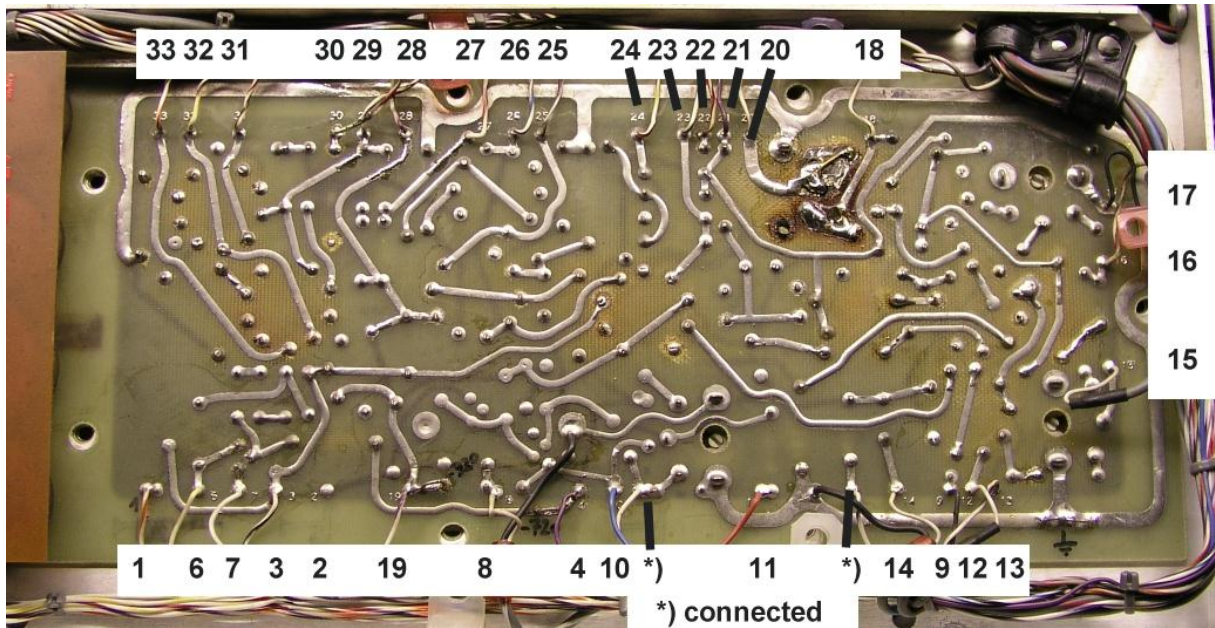

Picture 4: Layout of “old” circuit with pin numbers – don’t forget labeling !

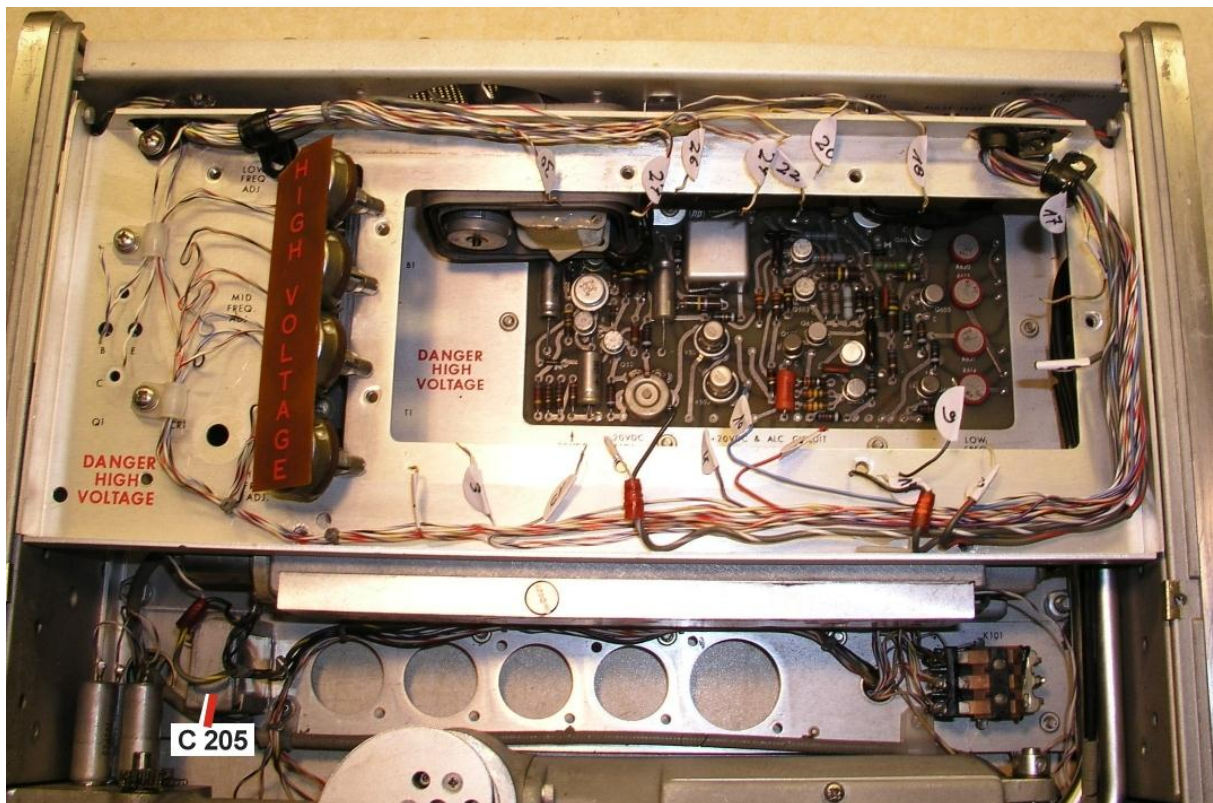


Picture 5: Removed HV-circuit, filament supply regulator and electrolytic capacitors  
(The “old” ALC-board can be seen)






Picture 6: The new HV-board

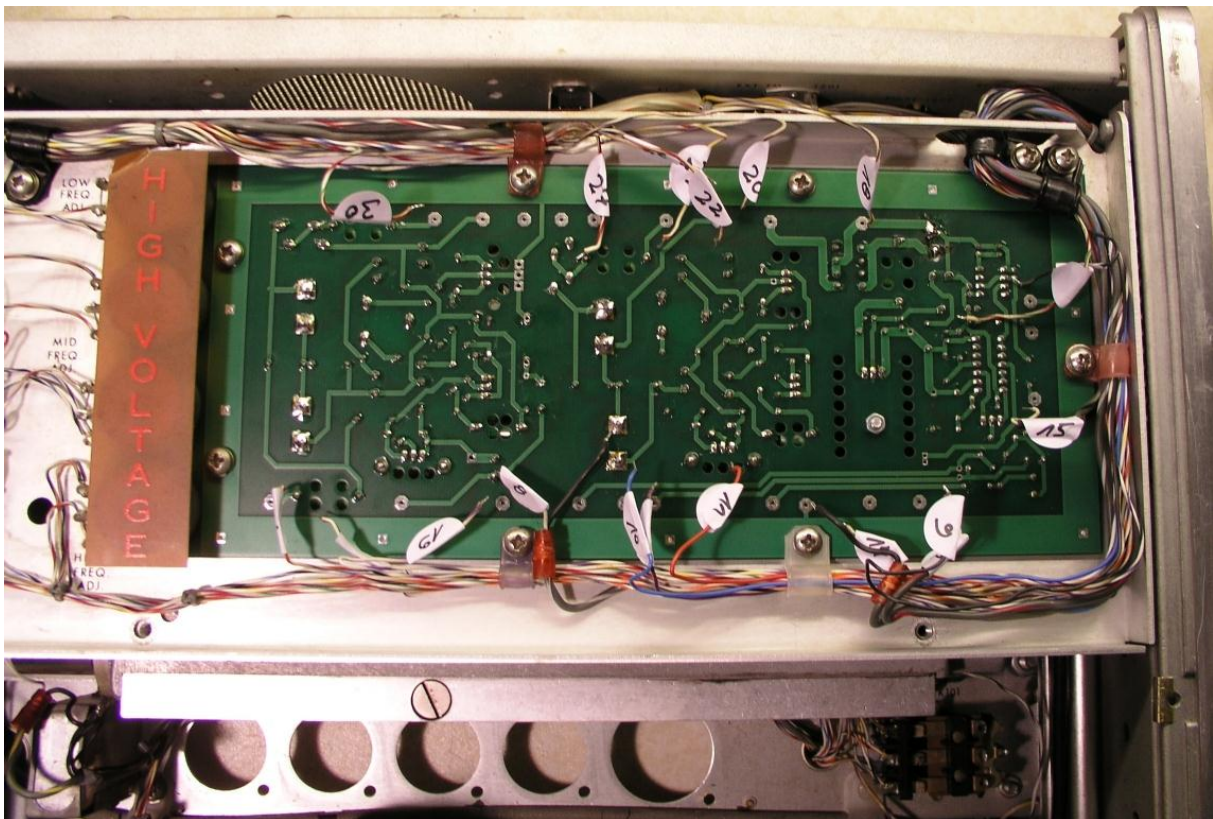


Picture 7: New HV-board before soldering




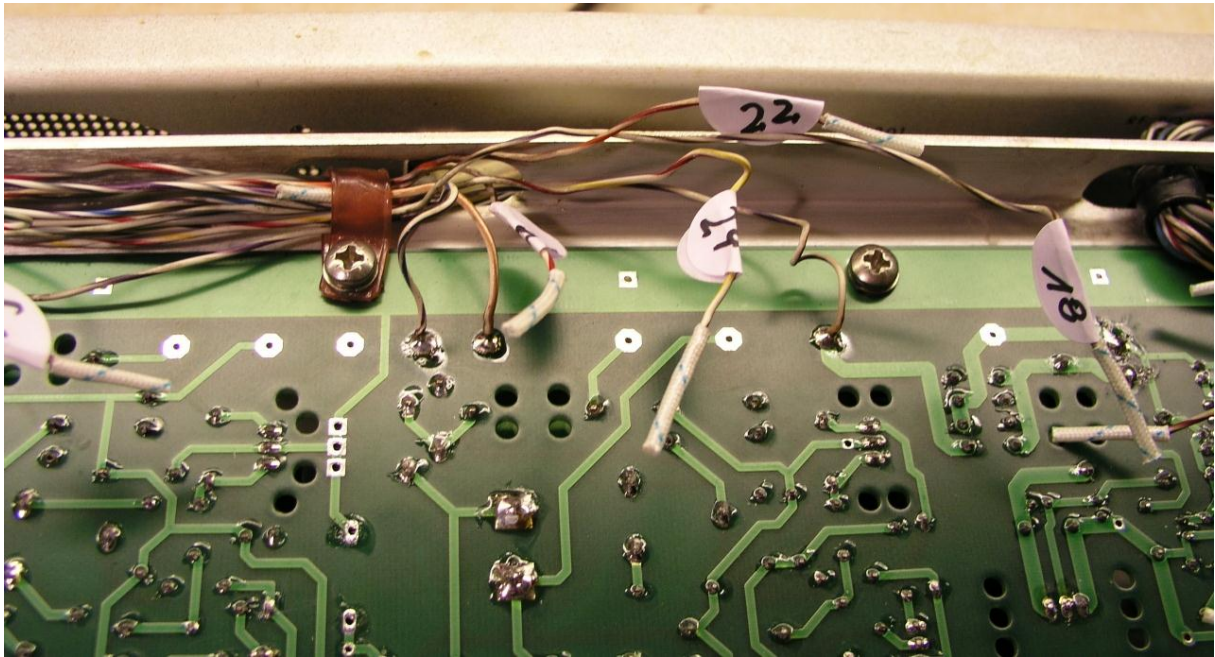


Picture 8: Some details

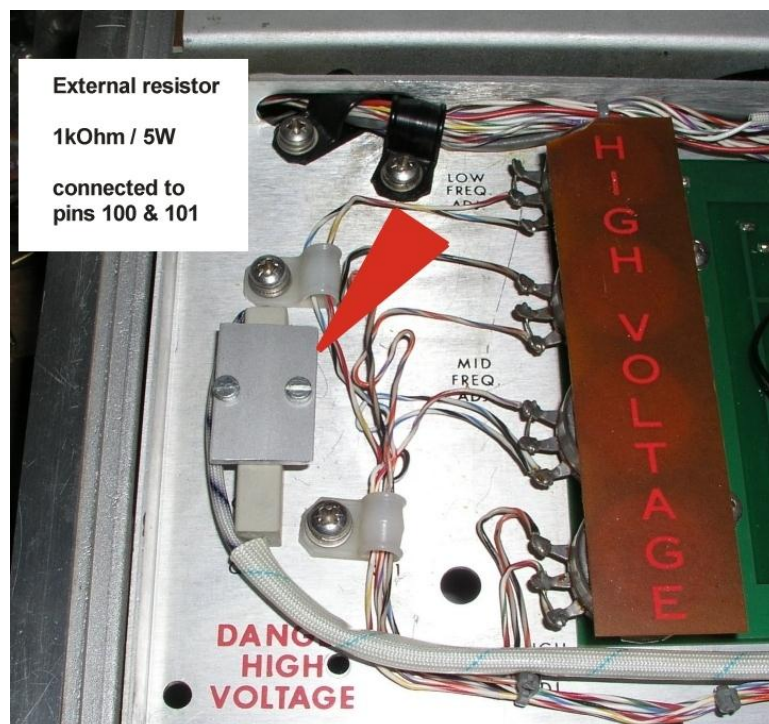

Picture 9: Additional external resistor (reduces heat dissipation in Q1)

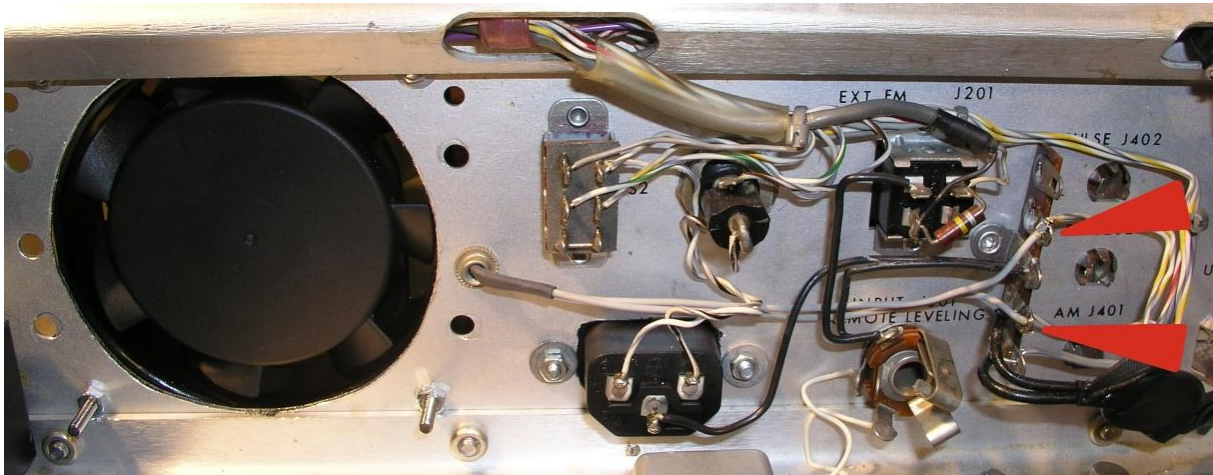

Picture 10: New fan 230VAC, connected to 115VAC for low speed

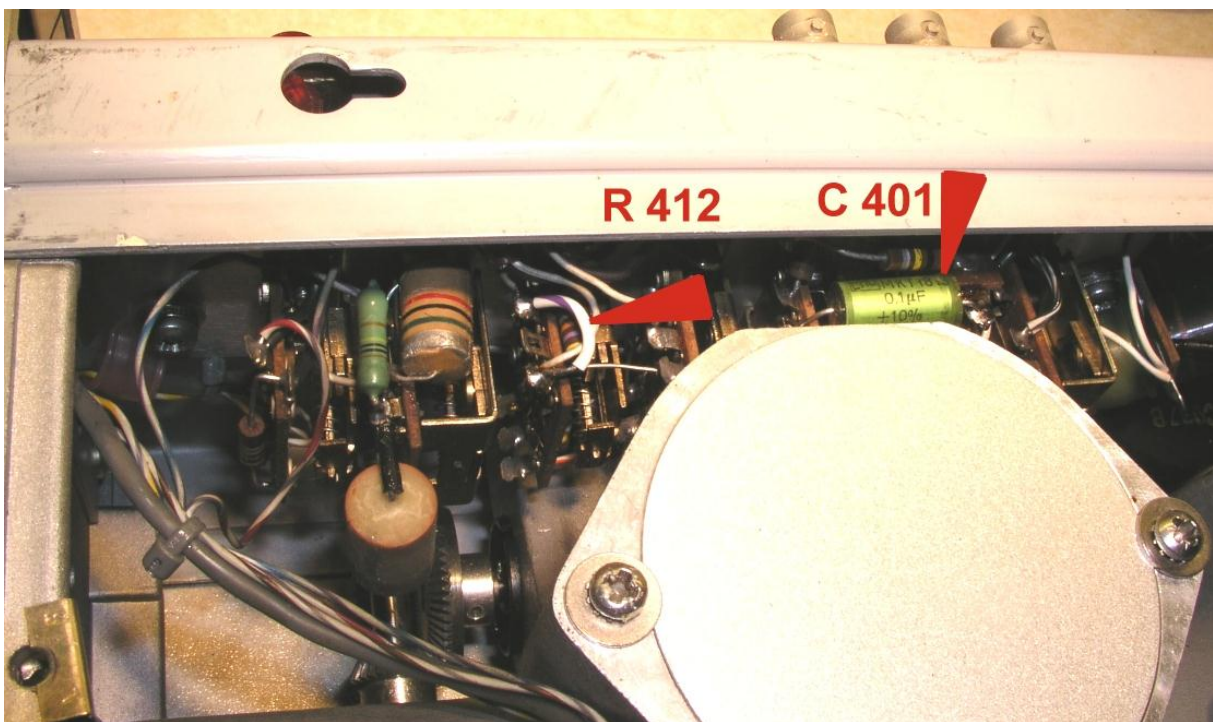

Picture 11: R412 bridged; C401 replaced by a better isolating type (MKT)

R412 has to be bridged to get a better frequency variation of the internal square wave generator.






Picture 12: Alignment of filament supply

The alignment of the modified generators can be done acc. to the manuals /1/.

Picture 13 shows the finished generator; the “old” ALC-circuit with transistors and nuvistors is still in use.



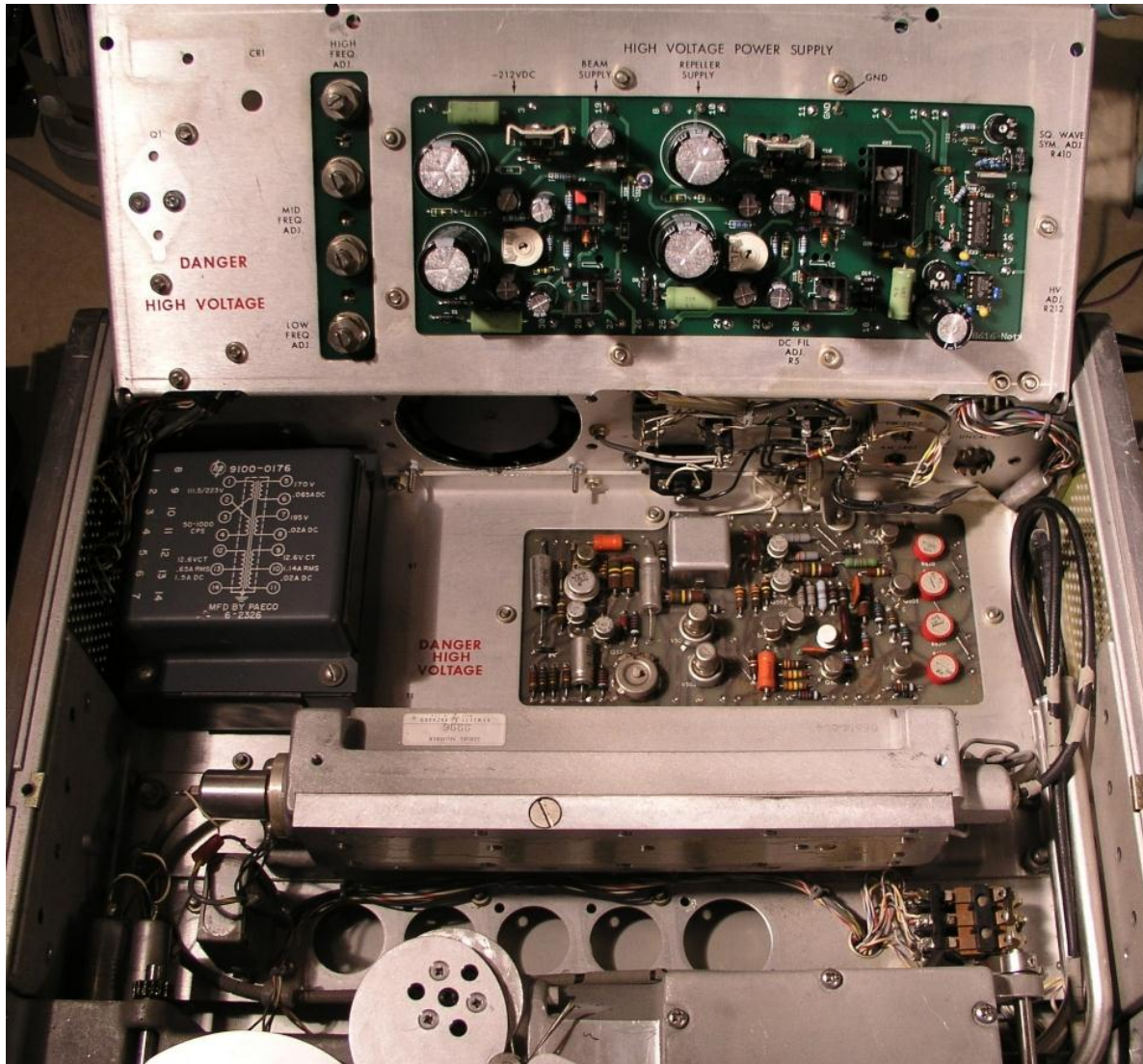

Picture 13: ALL IS DONE & READY

>> It was a crazy project and I don't recommend to do it ... smile <<

Please don't ask for PCB's – I don't have any and won't produce them!

/1/ Service and maintenance manuals of the HP8614 and HP8616

---

If you want to contact the author:

Stefan Steger, DL7MAJ, eMail: [dl7maj@darcl.de](mailto:dl7maj@darcl.de)

Homepage: [www.dl7maj.de](http://www.dl7maj.de)